

# MOSFET power losses and how they affect power-supply efficiency

by George Lakkas, Texas Instruments



Power-supply efficiency is a critical criterion for today's cloud-infrastructure hardware. The efficiency of the chosen power solutions relates to system power loss and the thermal performance of integrated circuits (ICs), printed circuit boards (PCBs), and other components, which determine the power-usage effectiveness of a data centre.

This article revisits some of the basic principles of power supplies and then addresses how MOSFETs – the power stage of any switching-voltage regulator – affect efficiency. For the linear regulator shown in Fig. 1, power loss and efficiency are defined by Eqs. 1 and 2.

$$\text{Power loss} = (V_{IN} - V_{OUT}) \times I_L \quad (1)$$

$$\text{Efficiency} = \frac{V_{OUT} \times I_L}{V_{IN} \times I_L} = \frac{V_{OUT}}{V_{IN}} \quad (2)$$

In the ideal switching regulator shown in Fig. 2, the current is zero when the switch is open and the power loss is zero, thus  $V_{IN}$  is being chopped. When the switch is closed, the voltage across it is zero and the power loss is also zero. An ideal switch implies

zero losses, thus offering 100% efficiency. However, components are not ideal, as is illustrated in the following examples.

An efficient switching regulator results in less heat dissipation, which reduces system cost and size for elements such as heat sinks, fans and their assembly. In battery-operated systems, less power loss means that these devices can use the same battery for a longer run time because the device pulls less current from the battery.

To consider the various factors that contribute to efficiency, the focus of this article is on the step-down (buck) DC/DC converter topology, which is the most popular switching-regulator topology in today's cloud infrastructure systems. Fig. 3 shows the key power-loss

contributors in a buck converter: conduction losses, switching losses, and static (quiescent) losses.

MOSFETs have a finite switching time, therefore, switching losses come from the dynamic voltages and currents the MOSFETs must handle during the time it takes to turn on or off.

Switching losses in the inductor come from the core and core losses. Gate-drive losses are also switching losses because they are required to turn the FETs on and off. For the control circuit, the quiescent current contributes to power loss; the faster the comparator, the higher the bias current. For the feedback circuit, the voltage divider, error amplifier and comparator bias currents

 


Fig. 1: Typical linear regulator.

 


Fig. 2: Ideal switching regulator.

 


Fig. 3: Power-loss contributors in a buck switching regulator.

 


Fig. 4: MOSFET conduction losses.

 


Fig. 5: MOSFET switching losses.

 


Fig. 6: Switch MOSFET gate losses.

 


Fig. 7: General gate losses.

 


Fig. 8: Total switch MOSFET losses.

 


Fig. 9: Rectifier MOSFET body-diode current.

contribute to power loss. Megaohm resistors cannot be used to reduce power loss because of the bias current into the feedback circuit. Fig. 4 shows a basic switching circuit and Eqn. 3 is used to calculate conduction losses for Q1 or Q2.

$$P_{CON} = R_{DS(on)} \times I_{QSW(RMS)}^2 \quad (3)$$

$$= R_{DS(on)} \times \frac{V_{OUT}}{V_{IN}} \times \left( I_{OUT}^2 + \frac{I_{RIPPLE}^2}{12} \right)$$

Note that  $R$  is the  $R_{DS(on)}$  of the selected MOSFET,  $I$  is the root-mean-square (RMS) current through the MOSFET, and that neither of these is a function of switching frequency. In general, a higher switching frequency and higher input voltage require a lower QG (gate charge) to cut down the switching losses in the switch MOSFET (Q1).

For a rectifier MOSFET (Q2), low  $R_{DS(on)}$  is most important, but don't ignore the gate power. Also, changing the MOSFET  $R_{DS(on)}$  changes the duty cycle ( $D$ ), which affects RMS currents and losses elsewhere. The inductor current also affects MOSFET conduction loss.

The high-side MOSFET (Q1) switching losses are evaluated first in Fig. 5 because they are more complex.

Relationships for Fig. 5 to derive loss equation:

$$E_{t1} = (V_{DS} \times I_D / 2) \times t_1,$$

$$E_{t2} = (V_{DS} / 2 \times I_D) \times t_2,$$

$$P_{SW} = 2 \times (E_{t1} + E_{t2}) \times f_{SW},$$

$$t_1 = Q_{GS2} / I_G,$$

$$t_2 = Q_{GD} / I_G,$$

$$V_{PLAT} = \text{Miller plateau},$$

$$V_{TH} = \text{Gate-to-source threshold voltage},$$

$$I_G = Cdv/dt,$$

$$Q = C \times V,$$

$$dt = t_1 \text{ or } t_2, \text{ and}$$

$V_{GS(actual)}$  is the actual gate-to-source drive voltage driving the MOSFET.

MOSFET switching losses are a function of load current and the power supply's switching frequency as shown by Eqn. 4.

$$P_{SW} = V_{IN} \times I_{OUT} \times f_{SW} \times \left( \frac{Q_{GS2} + Q_{GD}}{I_G} \right) \quad (4)$$

where  $V_{IN} = V_{DS}$  (drain-to-source voltage),  $I_{OUT} = I_D$  (drain current),  $f_{SW}$  is the switching

frequency,  $Q_{GS2}$  and  $Q_{GD}$  depend on the time the driver takes to charge the FET, and  $I_G$  is the gate current.

Switch-MOSFET gate losses can be caused by the energy required to charge the MOSFET gate. That is, the  $Q_{G(TOT)}$  at the gate voltage of the circuit. These are both turn-on and turn-off gate losses.

Most of the power is in the MOSFET gate driver. Gate-drive losses are frequency-dependent and are also a function of the gate capacitance of the MOSFETs. When turning the MOSFET on and off, the higher the switching frequency, the higher the gate-drive losses. This is another reason why efficiency goes down as the switching frequency goes up.

Larger MOSFETs with lower  $R_{DS(on)}$  provide lower conduction losses at the cost of higher gate capacitances, which results in higher gate-drive losses. These losses can be significant for power-supply controllers (with external MOSFETs) at very high switching frequencies in the multiple-megahertz region. There is no known method for calculating a "best"  $Q_G$  and  $R_{DS(on)}$  in a given situation, although figure-of-merit (FOM) numbers are typically mentioned in data sheets as  $(FOM = R_{DS(on)} \times Q_G)$ .

 


Fig. 10: Rectifier MOSFET gate driver and losses.

 


Fig. 11: Total rectifier MOSFET losses.

For the switch MOSFET shown in Fig. 6, a lower gate charge ( $Q_g$ ) in Eqn. 5 enables lower power loss and a faster switching time; however, this contributes to more parasitic turn-on of the rectifier MOSFET. A happy medium can be obtained in the design to accommodate these trade-offs.

$$P_{GATE} = Q_{G(TOT)} \times V_G \times f_{SW} \quad (5)$$

There are also general gate losses as shown in Fig. 7. The MOSFET effect on the gate-driver IC, or a pulse-width modulation (PWM) controller with an integrated gate driver, add to the power-dissipation losses.

As shown by Equation 6, gate-drive losses do not all occur on the MOSFET.

$$= R_{DRV} \times \frac{V_{G\_DRV} \times Q_{G(tot)} \times f_s}{2} \times \left( \frac{R_{GHI}}{R_{GHI} + R_G + R_{GI}} + \frac{R_{GLO}}{R_{GLO} + R_G + R_{GI}} \right) \quad (6)$$

where:

- $P_{DRV}$  is the total gate drive loss divided to calculate the driver loss,
- $R_{GHI}$  is turn on of the driver,
- $R_{GLO}$  is the turn off of the driver,
- Replacing  $R_{GHI}$  with  $R_G$  is the loss in the gate resistor.
- Replacing  $R_{GHI}$  with  $R_{GI}$  is the switching FET loss,
- Higher  $Q_g$  increases driver dissipation, and
- Adding external  $R_G$  reduces internal driver dissipation because it reduces the overall resistance path to the MOSFET gate.

Fig. 8 shows the various contributors that affect total switch MOSFET losses.

Now consider the rectifier (synchronous) MOSFET total and conduction losses. Power loss in a rectifier MOSFET consists of conduction

losses ( $P_{CON}$ ), body-diode conduction losses ( $P_{BD}$ ), and gate losses ( $P_{GATE}$ ).

There are no switching losses because of the bodydiode. The body diode conducts and the voltage across the FET is the diode voltage, which is zero. The body diode ensures zero-voltage switching per Eqn. 7.

$$P_{QSR} = P_{CON} + P_{BD} \times P_{GATE} \quad (7)$$

Conduction losses are simple  $I_2R$  losses when the MOSFET channel conducts per Eqn. 8.

$$P_{CON} = R_{DS(on)} \times \left[ 1 - \frac{V_{OUT}}{V_{IN}} - (t_{DLYUpLo} + t_{DLYUpUp}) \times f_{SW} \right] \times \left( I_{OUT}^2 + \frac{I_{RIPPLE}^2}{12} \right) \quad (8)$$

where:

- $R$  is the  $R_{DS(on)}$  of the selected MOSFET,
- $I$  is the RMS current through the MOSFET,
- $t_{DLYUpLo}$  is the delay between the upper MOSFET turning off and the lower MOSFET turning on, and
- $t_{DLYUpUp}$  is the delay between the lower MOSFET turning off and the upper MOSFET turning on.

The rectifier MOSFET also has body-diode losses. The average body-diode current can be calculated during dead time.

The blue waveform in Fig. 9 shows the dead time, which is the time between when the high-side FET turns off and the low-side FET (rectifier FET) turns on. We want the average current in the switching cycle. The output inductor ( $L$ ) dictates the slope of the dotted line,  $I_{BD1}$ ,  $I_{BD2}$ ,  $I_{BD3}$ . This slope is the average current through the body diode.

Eqns. 9a through 9e can be used to determine the body-diode current:

$$I_{BD(1)} = I_{BD(PK)} - \frac{V_0 \times t_{DLYUpLo}}{L} \quad (9a)$$

$$I_{BD(2)} = I_{BD(PK)} - I_{RIPPLE} + \frac{V_0 \times t_{DLYLoUp}}{L} \quad (9b)$$

$$I_{AVGUpLo} = I_{BD(PK)} - \frac{V_0 \times t_{DLYUpLo}}{2 \times L} \quad (9c)$$

$$I_{AVGLoUp} = I_{BD(PK)} - I_{RIPPLE} + \frac{V_0 \times t_{DLYLoUp}}{2 \times L} \quad (9d)$$

$$I_{BD(AVG)} = \left[ \left( I_{BD(PK)} - \frac{V_0 \times t_{DLYUpLo}}{2 \times L} \right) \times t_{DLYUpLo} + \left( I_{BD(PK)} - I_{RIPPLE} + \frac{V_0 \times t_{DLYLoUp}}{2 \times L} \right) \times t_{DLYLoUp} \right] \times f_{sw} \quad (9e)$$

Eqn. 10 can be used to approximate the body-diode power loss.

$$P_{BD} = V_F \times I_{OUT} \times (t_{DLYUpLo} + t_{DLYLoUp}) \times f_{sw} \quad (10)$$

The final consideration in Fig. 10 is for the gate losses of the rectifier MOSFET (Q2). Gate losses are calculated in the same manner as with the switch MOSFET. Losses can be significant because of a higher gate charge.

Fig. 11 shows the various contributors that affect total losses attributed to the rectifier MOSFET.

## Conclusion

The efficiency of a synchronous step-down power converter with integrated or external MOSFETs can be optimised when the designer understands the parameters that affect efficiency and the specifications to look for in data sheets.

In the absence of an ideal power converter, the designer has to make trade-offs and optimise the parameters that affect power-supply efficiency.

**Contact Erich Nast, Avnet South Africa, Tel 011 319-8600, erich.nast@avnet.eu**